 


## More Complex Gates

$$F = \overline{AB + CD} \Rightarrow N_{\text{tree}} \text{ will provide 0's, } P_{\text{tree}} \text{ will provide 1's}$$

$$\text{0's of function } F \text{ is } \overline{F}, \Rightarrow \overline{F} = \overline{\overline{AB + CD}} = AB + CD$$

*n*MOS transistors need high true inputs, so it is desirable for all input variables to be high true, just as above.




Likewise, a  $P_{\text{tree}}$  will provide 1's.

$$F = \overline{AB + CD}, \quad \text{need a form involving } \overline{A}, \overline{B}, \overline{C}, \overline{D}$$

Apply DeMorgan's Theorem:

$$F = \overline{AB} \cdot \overline{CD} = (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$

Implementation  $\Rightarrow$

 

Can also use K-maps:

$$F = \overline{AB} + CD$$

	AB			
	1	1	0	1
1	1	1	0	1
0	0	0	0	0
1	1	0	1	1

For  $N_{tree}$ , minimize 0's; for  $P_{tree}$ , minimize 1's


	AB			
		0		
		0		
0	0	0	0	
		0		

$$N_{tree} = AB + CD$$

	AB			
	1	1		1
	1	1		1
	1	1		1

$$\begin{aligned}
 P_{tree} &= \overline{A} \cdot \overline{C} + \overline{A} \cdot \overline{D} + \overline{B} \cdot \overline{C} + \overline{B} \cdot \overline{D} \\
 &= \overline{A} (\overline{C} + \overline{D}) + \overline{B} (\overline{C} + \overline{D}) \\
 &= (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})
 \end{aligned}$$


# Tri State Inverter

 

EN	I	O
0	X	Z
1	0	1
1	1	0


"Z" is high impedance state

Implementation? Here is one method:

 


6 transistors total

Alternate representations:

 


or

 

where the connection for  $\overline{EN}$  is understood or implied,  $\overline{EN}$  still needs to somehow be provided in the physical circuit

# Transmission Pass Gate Logic

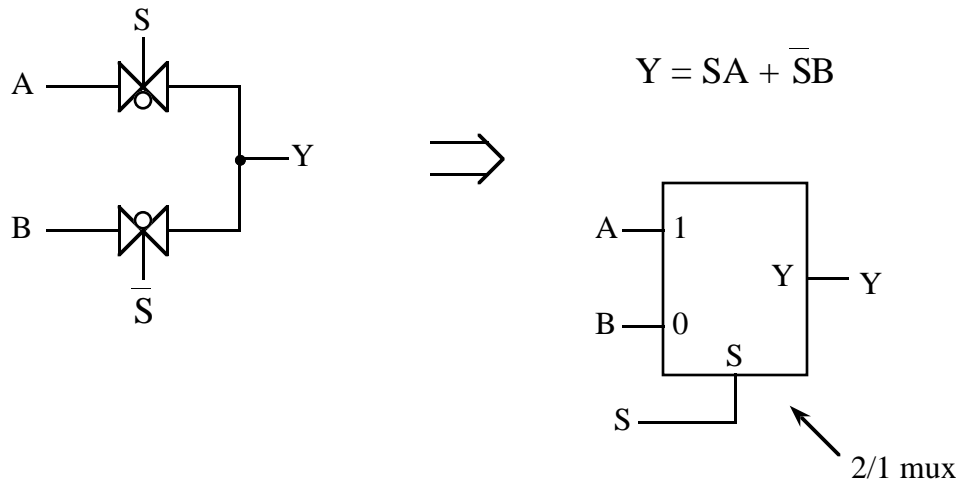


Will require

$$(4 \text{ transistors for two pass gates}) + (2 \text{ transistors for inversion of } S) = 6 \text{ transistors total}$$

This technique uses less transistors than a design using normal gates, but is non-restoring. Pass gate logic has no drive capability. Drive comes from original A, B inputs.


A D-Latch using transmission gates:

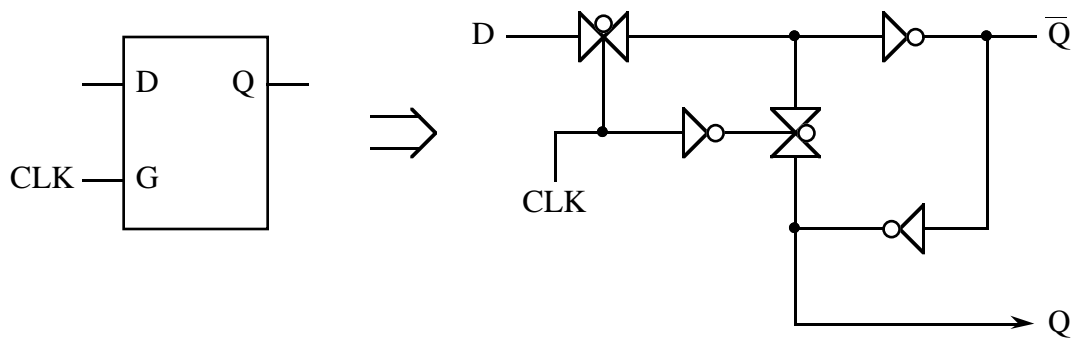


when  $CLK = 1,$   $Q = D$   
 $CLK = 0,$   $Q = Q_{old}$

Recall flip-flop construction from CAD course (edge triggered device) —  
 → two latches in a master-slave arrangement are required


Falling edge triggered

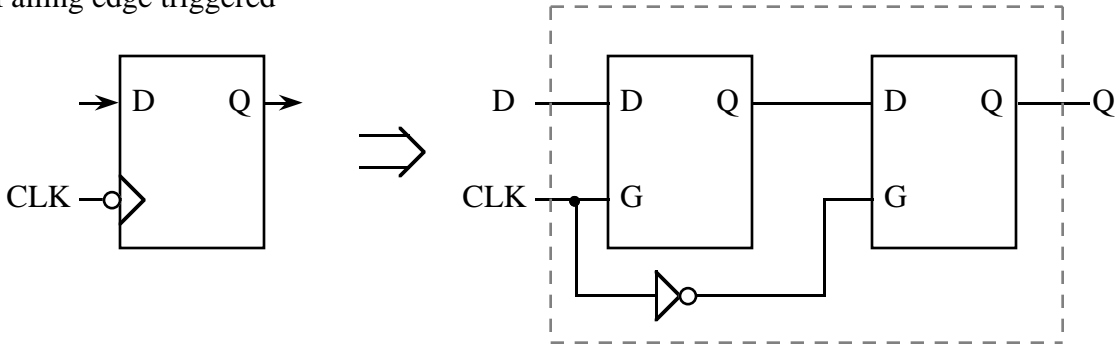

Rising edge triggered

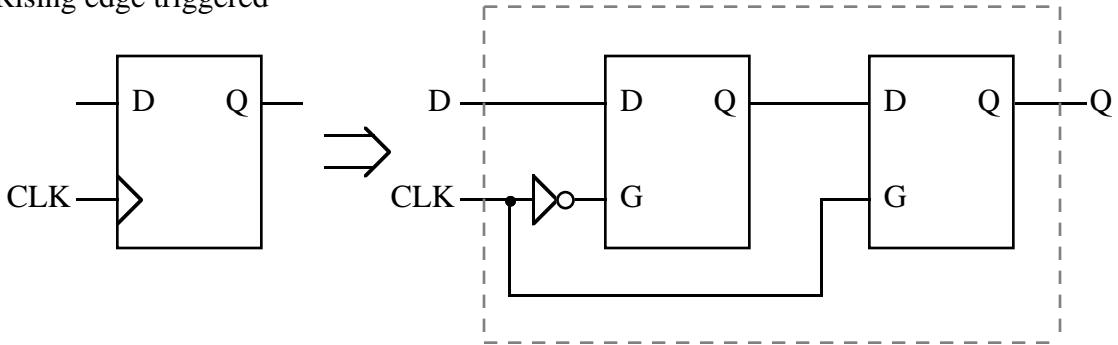

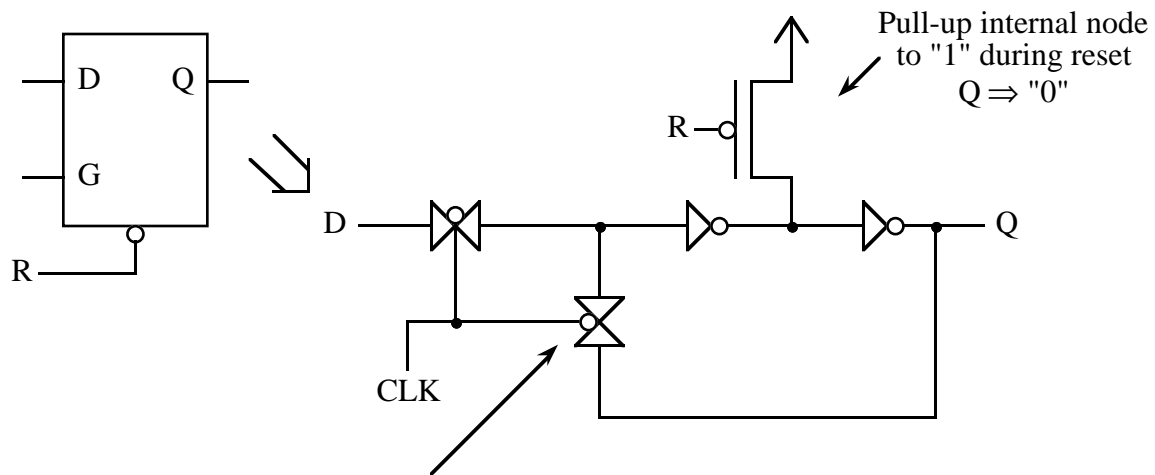
How would a D-Latch with an asynchronous reset be implemented?



Note: when connected to inverted terminal of transmission gate, then the inverter is implied

## Introduction to Static Load Inverters

1)

 

When  $I = 1$ , inverter dissipates static power.


Switching point of inverter depends on ratio of  $R$  to  $R_{ON}$  (on resistance of  $n$ MOS device).

$$V_{OH} = 5V,$$

$$V_{OL} \approx 0V, \text{ depends on ratio of } R/R_{On}$$

Note: output can swing from 0V to 5V ( $V_{dd}$ )

2)

 

Load is enhancement-mode  $n$ MOS device.

Again, static power dissipation occurs when  $I = 1$ .


Note: output swings from  $\approx 0V$  to  $(V_{dd} - V_{Tn})$

Using a transistor as a load tends to require much less silicon area than a resistor.

$$V_{OH} = V_{dd} - V_{Tn},$$


$$V_{OL} \approx 0V, \text{ depending on ratio of } R_{ON} \text{ of two enhancement devices}$$

Depletion-mode *n*MOS

 

*n*MOS device with  $V_{Tn} < 0V$  (negative threshold voltage). Device is always conducting if  $V_{GS} > 0V$ .

3)

 

$V_{GS} = 0V$  always


Load device is always on, looks like a load resistor.

Dissipates static power when  $I = 1$

$V_{OH} = 5V$ ;  $V_{OL} \approx 0V$ , depending on ratio of  $R_{ON,dep}$  to  $R_{ON,enh}$ .

Depletion-mode devices were used before it was economical to put both *p*-type and *n*-type devices on the same die.

4) *p*MOS device as static load

 


Here also the load device is always on (conducting).

Dissipates static power when  $I = 1$ .

$V_{OH} = 5V$ ;  $V_{OL} \approx 0V$ , depending on ratio of  $R_{ON,p}$  to  $R_{ON,n}$

## Basic MOS Device Equations

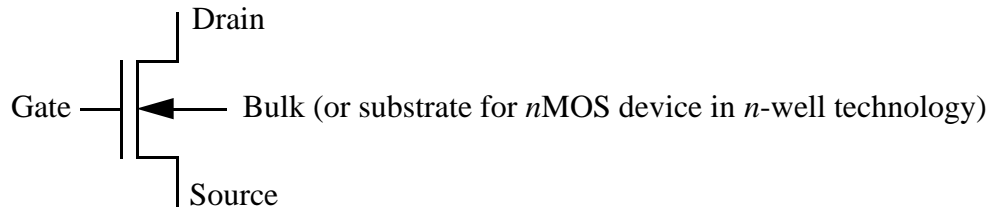

The  $n$ MOS device is a *four* terminal device: Gate, Drain, Source, Bulk.

Bulk (substrate) terminal is normally ignored at schematic level, usually tied to ground for the  $n$ MOS case. In analog applications, however, the bulk terminal may not be ignored.

Gate controls channel formation for conduction between Drain and Source. Drain at higher potential than Source — Source usually tied to GND to act as pull-down ( $n$ MOS).

Three regions of operations — first-order (*ideal*) equations:

### Cutoff region

$$I_D = 0A \quad V_{GS} \leq V_{Tn} \text{ (nMOS threshold voltage)}$$

### Linear region

$$I_D = \beta \left( (V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad 0 < V_{DS} < V_{GS} - V_{Tn}$$

Note:  $I_D$  is linear with respect to  $(V_{GS} - V_{Tn})$  only when  $\frac{V_{DS}^2}{2}$  is small.

### Saturation region

$$I_D = \frac{\beta}{2} (V_{GS} - V_{Tn})^2 \quad 0 < V_{GS} - V_{Tn} < V_{DS}$$



Device parameters:

$\beta$  = transistor gain factor, dependent on process parameters and device geometry

$$\beta = \left( \frac{\mu\epsilon}{t_{ox}} \right) \left( \frac{W}{L} \right)$$

↙ process dependent, constant  
 ↘ under control of the designer

As  $W/L$  increases, effective  $R_{ON}$  of device decreases

$\mu$  = surface mobility of the carriers in the channel

$\epsilon$  = permittivity of the gate insulator

$t_{ox}$  = thickness of the gate insulator

See Figure 2.5, 2.8 concerning  $\mu$ ,  $\epsilon$ , and  $t_{ox}$



SPICE represents  $\beta$  by a factor given by

$$K' = \mu C_{ox} = \mu \frac{\epsilon}{t_{ox}} = \mathbf{KP}$$

So,

$$I_D = \frac{K'}{2} \frac{W}{L} (V_{GS} - V_{Tn})^2; \quad \text{saturation region}$$

## VI characteristic

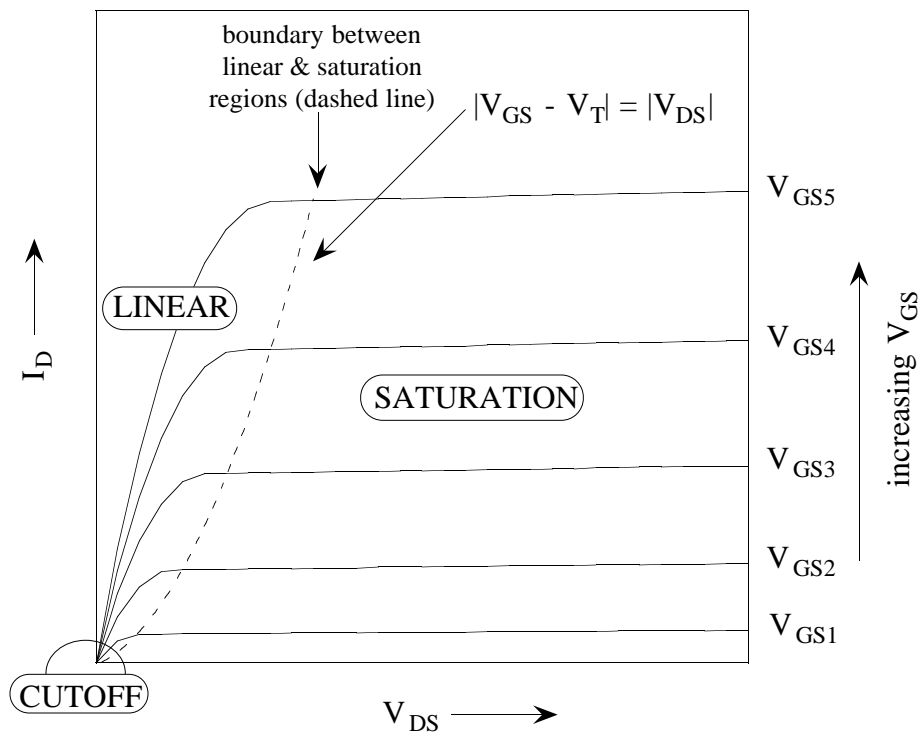 

Things to note:

In the "linear" region,  $I_D$  becomes less and less linear with  $V_{GS}$  as  $V_{DS}$  becomes large. This is because the  $\frac{V_{DS}^2}{2}$  term in the linear region grows large.


Higher  $V_{GS}$  values increase channel conductance allowing for higher values of  $I_D$  for a given  $V_{DS}$ .

## Predicting $I_D$ values with ideal equations

In saturation region,

$$I_D = K' \left( \frac{W}{L} \right) \frac{(V_{GS} - V_T)^2}{2}$$

If we have

 

then we can calculate  $I_D$  based on  $V_{in}$ ,  $K'$ ,  $V_T$  (MOSFET parameters).

In specifying  $W$ ,  $L$  values, these are often given in a dimensionless unit called lambda.

When mapping the transistor schematic/layout to a particular technology, the actual  $W$ ,  $L$  will be calculated as:

$$\begin{aligned} W' \text{ (actual, microns } (\mu)) &= W \times \text{lambda (microns)} \\ L' \text{ (actual, microns)} &= L \times \text{lambda (microns)} \end{aligned}$$

So lambda is a scaling factor. Note that the ratio  $\frac{W}{L}$  is what is important, and that

$$\frac{W'}{L'} = \frac{W \times \text{lambda}}{L \times \text{lambda}} = \frac{W}{L} \cdot$$

Scaling factor lambda allows transistor  $\frac{W}{L}$  values specified in schematics to be technology independent.

For MOSIS foundry vendors,


2.0 $\mu$  technology  $\Rightarrow$  lambda = 1.0

1.2 $\mu$  technology  $\Rightarrow$  lambda = 0.6

0.8 $\mu$  technology  $\Rightarrow$  lambda = 0.4.

Note, however, that lambda *is not* always  $\frac{1}{2}$  technology minimum feature size (line width). Scaling factor lambda *is* foundry/silicon vendor dependent.


In schematic,

 

mapped to 1.2 $\mu$  technology,

$$\frac{W}{L} = \frac{10.8\mu}{1.2\mu}$$

*n*MOSFET layout:

 

In digital logic, typically will draw all transistors with the minimum gate length ( $= 2 \times \lambda$ ) and vary the width.

Larger  $W \Rightarrow$  larger transconductance (more current flow for given gate voltage), higher gate capacitance

During fabrication process, the actual width and length of the channel can be *reduced* by diffusion from the bulk, source, and drain into the device channel.

SPICE has some MOSFET model parameters to account for this effect,  $L_D$  and  $W_D$ , where the actual the actual length and width is calculated as

$$L_{\text{effective}} = L_{\text{drawn}} - 2 \times L_D$$

$$W_{\text{effective}} = W_{\text{drawn}} - 2 \times W_D$$

If  $L_D$ ,  $W_D$  parameters not specified in the model, then SPICE assumes they are 0.