

Concurrent Signal Assignment Statements

Outline

1. Combinational versus sequential circuit
2. Simple signal assignment statement
3. Conditional signal assignment statement
4. Selected signal assignment statement
5. Conditional vs. selected signal assignment


1. Combinational vs. sequential circuit

- Combinational circuit:
 - No internal state
 - Output is a function of inputs only
 - No latches/FFs or closed feedback loop
- Sequential circuit:
 - With internal state
 - Output is a function of inputs and internal state
- Sequential circuit to be discussed later

 2. Simple signal assignment statement

- Simple signal assignment is a special case of conditional signal assignment
- Syntax:
signal_name <= projected_waveform;
- E.g.,
y <= a + b + 1 **after** 10 ns;
- Timing info ignored in synthesis and δ -delay is used:
signal_name <= value_expression

- E.g.,
status <= '1';
even <= (p1 **and** p2) **or** (p3 **and** p4);
arith_out <= a + b + c - 1;
- Implementation of last statement



Signal assignment statement with a closed feedback loop

- a signal appears in both sides of a concurrent assignment statement
- E.g.,
 $q \leq ((\text{not } q) \text{ and } (\text{not } \text{en})) \text{ or } (d \text{ and } \text{en});$
- Syntactically correct
- Form a closed feedback loop
- Should be avoided

3. Conditional signal assignment statement

- Syntax
- Examples
- Conceptual implementation
- Detailed implementation examples

Syntax

- Simplified syntax:

signal_name

```
<= value_expr_1 when boolean_expr_1 else  
value_expr_2 when boolean_expr_2 else  
value_expr_3 when boolean_expr_3 else  
...  
value_expr_n
```

E.g., 4-to-1 mux

- Function table:

input		output
s		x
0	0	a
0	1	b
1	0	c
1	1	d

```

library ieee;
use ieee.std_logic_1164.all;
entity mux4 is
    port(
        a,b,c,d: in std_logic_vector(7 downto 0);
        s: in std_logic_vector(1 downto 0);
        x: out std_logic_vector(7 downto 0)
    );
end mux4 ;
architecture cond_arch of mux4 is
begin
    x <= a when (s="00") else
        b when (s="01") else
        c when (s="10") else
        d;
end cond_arch;

```

E.g., 2-to-2² binary decoder

- Function table:

<hr/>	
input	output
s	x
<hr/>	
0 0	0001
0 1	0010
1 0	0100
1 1	1000
<hr/>	

```

library ieee;
use ieee.std_logic_1164.all;
entity decoder4 is
    port(
        s: in std_logic_vector(1 downto 0);
        x: out std_logic_vector(3 downto 0)
    );
end decoder4 ;
architecture cond_arch of decoder4 is
begin
    x <= "0001" when (s="00") else
        "0010" when (s="01") else
        "0100" when (s="10") else
        "1000";
end cond_arch;

```

E.g., 4-to-2 priority encoder

- Function table:

<hr/>			
input		output	
r		code	active
<hr/>			
1	---	11	1
0	1--	10	1
0	01-	01	1
0	001	00	1
0	000	00	0
<hr/>			

```

library ieee;
use ieee.std_logic_1164.all;
entity prio_encoder42 is
    port(
        r: in std_logic_vector(3 downto 0);
        code: out std_logic_vector(1 downto 0);
        active: out std_logic
    );
end prio_encoder42;
architecture cond_arch of prio_encoder42 is
begin
    code <= "11" when (r(3)='1') else
        "10" when (r(2)='1') else
        "01" when (r(1)='1') else
        "00";
    active <= r(3) or r(2) or r(1) or r(0);
end cond_arch ;

```

E.g., simple ALU

- Function table:

input ctrl	output result
0 --	src0 + 1
1 0 0	src0 + src1
1 0 1	src0 - src1
1 1 0	src0 and src1
1 1 1	src0 or src1


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity simple_alu is
    port(
        ctrl: in std_logic_vector(2 downto 0);
        src0, src1: in std_logic_vector(7 downto 0);
        result: out std_logic_vector(7 downto 0)
    );
end simple_alu ;

architecture cond_arch of simple_alu is
    signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
    inc <= std_logic_vector(signed(src0)+1);
    sum <= std_logic_vector(signed(src0)+signed(src1));
    diff <= std_logic_vector(signed(src0)-signed(src1));
    result <= inc when ctrl(2)='0' else
        sum when ctrl(1 downto 0)="00" else
        diff when ctrl(1 downto 0)="01" else
        src0 and src1 when ctrl(1 downto 0)="10" else
        src0 or src1;
end cond_arch;

```

Conceptual implementation

- Syntax:


signal_name

```
<= value_expr_1 when boolean_expr_1 else  
    value_expr_2 when boolean_expr_2 else  
    value_expr_3 when boolean_expr_3 else  
    ...  
    value_expr_n;
```


- Evaluation in ascending order
- Achieved by “priority-routing network”
- Top value expression has a “higher priority”

2-to-1 “abstract” mux

 
- sel has a data type of boolean
- If sel is true, the input from “T” port is connected to output.
- If sel is false, the input from “F” port is connected to output.



 
```
signal_name <= value_expr_1 when boolean_expr_1 else  
               value_expr_2;
```





 
```
signal_name <= value_expr_1 when boolean_expr_1 else  
value_expr_2 when boolean_expr_2 else  
value_expr_3 when boolean_expr_3 else  
value_expr_4;
```



 

Detailed implementation examples


- 2-to-1 mux

   


- E.g.,


```

       signal a,b,y: std_logic;
      y <= '0' when a=b else
          '1';
      
```





input		output
a	b	a=b
0	0	1
0	1	0
1	0	0
1	1	1

 

- E.g.,
 
```
signal a,b,c,x,y,r: std_logic;  
. . .  
r <= a when x=y else  
    b when x>y else  
    c;
```




 


- E.g.,

```

. . .
signal a,b,r: unsigned(7 downto 0);
signal x,y: unsigned(3 downto 0);
. . .
r <= a+b when x+y>1 else
    a-b-1 when x>y and y!=0 else
    a+1;

```

 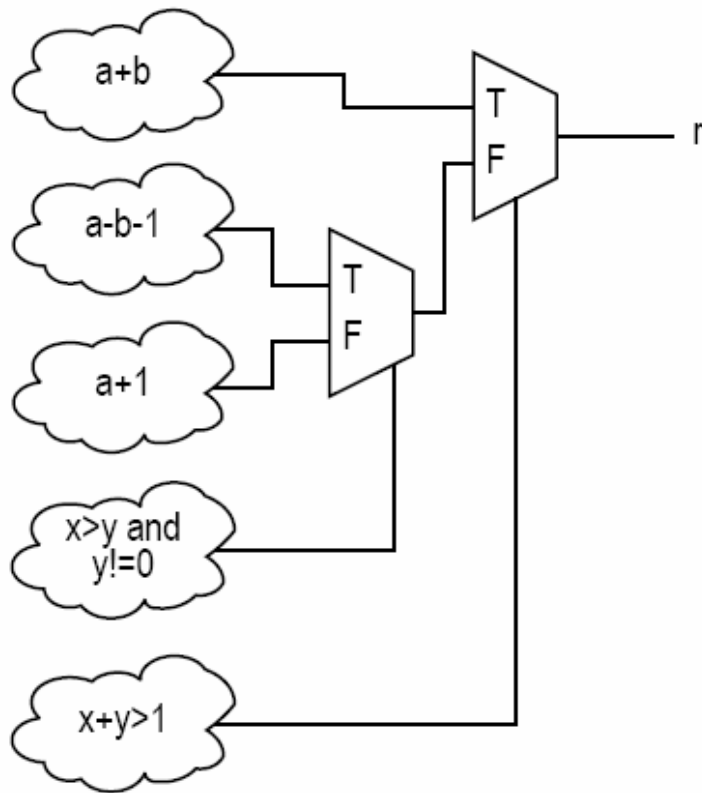

4. Selected signal assignment statement

- Syntax
- Examples
- Conceptual implementation
- Detailed implementation examples

Syntax

- Simplified syntax:

with select_expression **select**

signal_name <=

value_expr_1 **when** choice_1,

value_expr_2 **when** choice_2,

value_expr_3 **when** choice_3,

...

value_expr_n **when** choice_n;

- `select_expression`
 - Discrete type or 1-D array
 - With finite possible values
- `choice_i`
 - A value of the data type
- Choices must be
 - mutually exclusive
 - all inclusive
 - **others** can be used as last `choice_i`

E.g., 4-to-1 mux

architecture sel_arch of mux4 is

begin

with s select

x <= a when "00",

b when "01",

c when "10",

d when others;

end sel_arch ;

input	output
s	x
00	a
01	b
10	c
11	d

- Can “11” be used to replace **others**?

```
with s select  
  x <= a when "00",  
    b when "01",  
    c when "10",  
    d when "11";  
- . -
```


E.g., 2-to-2² binary decoder

`architecture sel_arch of decoder4 is
begin`

`with sel select`

`x <= "0001" when "00",`

`"0010" when "01",`

`"0100" when "10",`

`"1000" when others;`

`end sel_arch ;`

input s	output x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

E.g., 4-to-2 priority encoder

```
architecture sel_arch of prio_encoder42 is
begin
  with r select
    code <= "11" when "1000" | "1001" | "1010" | "1011" |
                    "1100" | "1101" | "1110" | "1111",
           "10" when "0100" | "0101" | "0110" | "0111",
           "01" when "0010" | "0011",
           "00" when others;
  active <= r(3) or r(2) or r(1) or r(0);
end sel_arch;
```

input	output	
r	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

- Can we use '-'?

with a select

```
x <= "11" when "1---",  
     "10" when "01--",  
     "01" when "001-",  
     "00" when others;
```

E.g., simple ALU

```
architecture sel_arch of simple_alu is
    signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
    inc <= std_logic_vector(signed(src0)+1);
    sum <= std_logic_vector(signed(src0)+signed(src1));
    diff <= std_logic_vector(signed(src0)-signed(src1));
    with ctrl select
        result <= inc          when "000"|"001"|"010"|"011",
                sum           when "100",
                diff          when "101",
                src0 and src1 when "110",
                src0 or src1  when others;
end sel_arch;
```

input ctrl	output result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1


E.g., Truth table

```
library ieee;
use ieee.std_logic_1164.all;
entity truth_table is
    port (
        a,b: in    std_logic;
        y: out    std_logic
    );
end truth_table;
architecture a of truth_table is
    signal tmp: std_logic_vector(1 downto 0);
begin
    tmp <= a & b;
    with tmp select
        y <= '0' when "00",
           '1' when "01",
           '1' when "10",
           '1' when others; -- "11"
end a;
```

<hr/>	
input	output
a b	y
<hr/>	
0 0	0
0 1	1
1 0	1
1 1	1
<hr/>	


Conceptual implementation

 - Achieved by a multiplexing circuit
- Abstract $(k+1)$ -to-1 multiplexer
 - sel is with a data type of $(k+1)$ values:
 $c_0, c_1, c_2, \dots, c_k$




- `select_expression` is with a data type of 5 values: `c0`, `c1`, `c2`, `c3`, `c4`
 
```
with select_expression select  
    sig <= value_expr_0 when c0 ,  
        value_expr_1 when c1 ,  
        value_expr_n when others ;
```




Detailed implementation examples

- 4-to-1 mux

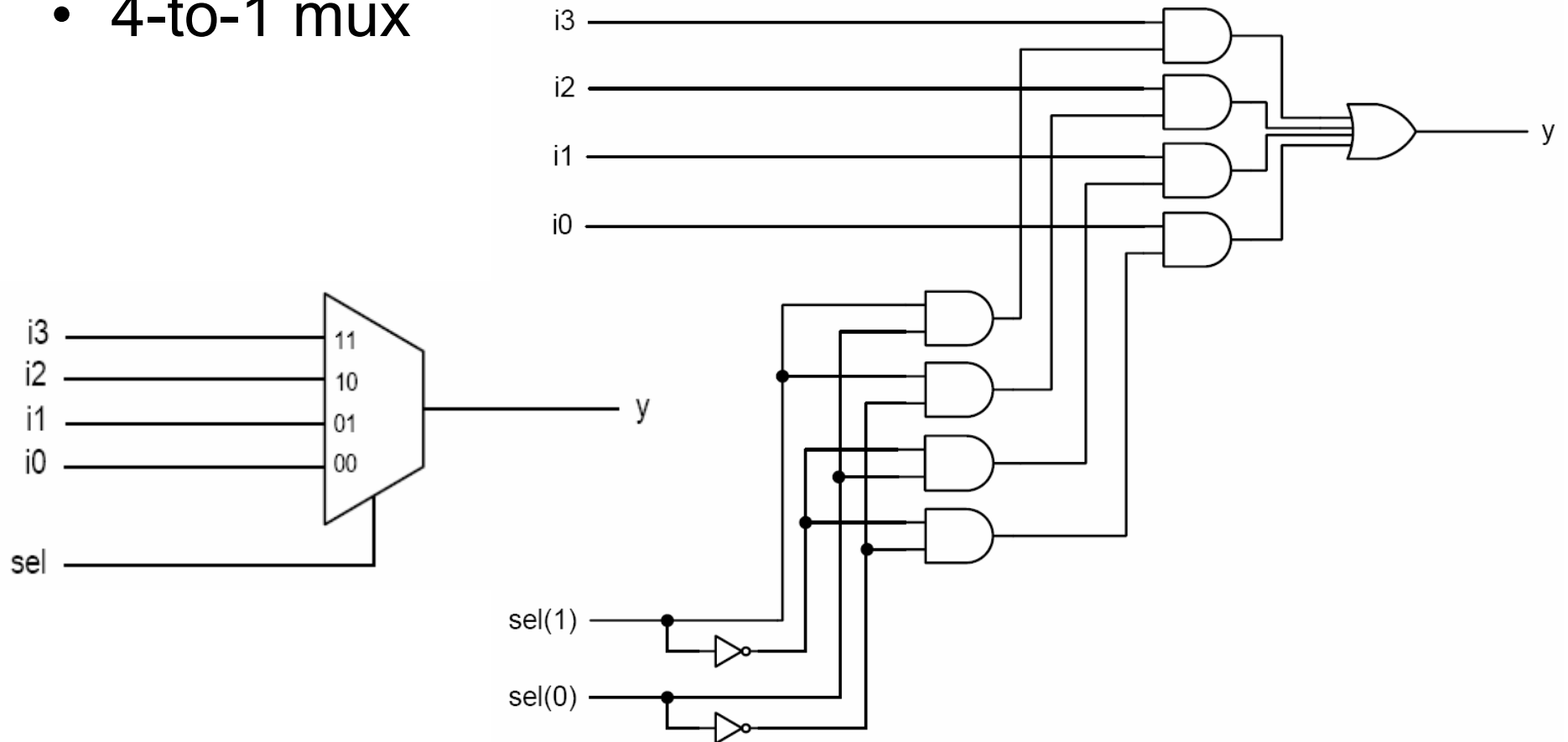

• E.g.,
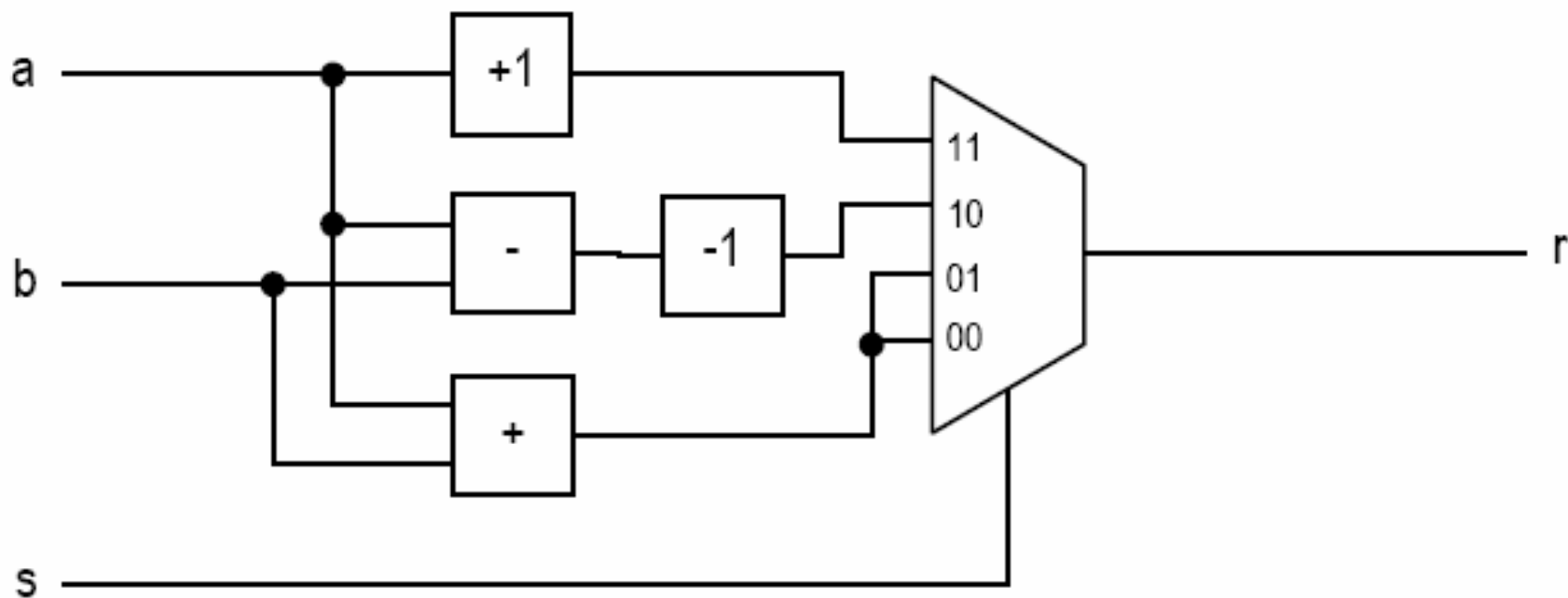
```
signal a,b,r: unsigned(7 downto 0);  
signal s: std_logic_vector(1 downto 0);  
.  
.  
.  
with s select  
    r <= a+1    when "11",  
        a-b-1  when "10",  
        a+b    when others;
```



3. Conditional vs. selected signal assignment

- Conversion between conditional vs. selected signal assignment
- Comparison

From selected assignment to conditional assignment

```
with sel select
```

```
    sig <= value_expr_0 when c0,  
          value_expr_1 when c1|c3|c5,  
          value_expr_2 when c2|c4,  
          value_expr_n when others;
```

```
sig <=
```

```
value_expr_0 when (sel=c0) else  
value_expr_1 when (sel=c1) or (sel=c3) or (sel=c5) else  
value_expr_2 when (sel=c2) or (sel=c4) else  
value_expr_n;
```

From conditional assignment to selected assignment

```
sig <= value_expr_0 when bool_exp_0 else
      value_expr_1 when bool_exp_1 else
      value_expr_2 when bool_exp_2 else
      value_expr_n;
```

```
sel(2) <= '1' when bool_exp_0 else '0';
sel(1) <= '1' when bool_exp_1 else '0';
sel(0) <= '1' when bool_exp_2 else '0';
with sel select
    sig <= value_expr_0 when "100"|"101"|"110"|"111",
          value_expr_1 when "010"|"011",
          value_expr_2 when "001",
          value_expr_n when others;
```

Comparison

- Selected signal assignment:
 - good match for a circuit described by a functional table
 - E.g., binary decoder, multiplexer
 - Less effective when an input pattern is given a preferential treatment

- Conditional signal assignment:
 - good match for a circuit a circuit that needs to give preferential treatment for certain conditions or to prioritize the operations
 - E.g., priority encoder
 - Can handle complicated conditions. e.g.,

```
pc_next <=
    pc_reg + offset when (state=jump and a=b) else
    pc_reg + 1 when (state=skip and flag='1') else
    . . .
```

– May “over-specify” for a functional table based circuit.

– E.g., mux

```
x <= a when (s="00") else
      b when (s="01") else
      c when (s="10") else
      d;
```

```
x <= c when (s="10") else
      a when (s="00") else
      b when (s="01") else
      d;
```

```
x <= c when (s="10") else
      b when (s="01") else
      a when (s="00") else
      d;
```