



High Speed Digital Circuit Lab

PIC16C5x :Verilog Example

High Speed Digital Circuit Lab.
Kyungpook National University

Contents

- PIC16C5x Spec.
- Refine Internal Architecture
 - Instruction Decoder
 - Program Counter
 - ALU
 - Registers
- Verification
- Synthesis
- Summary



High Speed Digital Circuit Lab

1

PIC16c5x Spec.

- Harvard Architecture
 - Program : 12bit X 2^{11} Data : 8bit X 72
- 33 instructions
 - 31 instructions available (except tri,clrwdt)
- Two level deep stack
- Direct, indirect and relative data/instruction addressing mode



High Speed Digital Circuit Lab

2

Instruction Format

- Byte-oriented register file operations

11	6	5	4	0
OPCODE		d		f(File #)
- Bit-oriented register file operations

11	8	7	5	4	0
OPCODE		b(BIT #)		f(File #)	
- Literal and control operations (except GOTO)

11	8	7	0
OPCODE		k(literal)	
- Literal and control operations-GOTO instruction


11	9	8	0
OPCODE		Long k(literal)	



High Speed Digital Circuit Lab

3


Internal Architecture

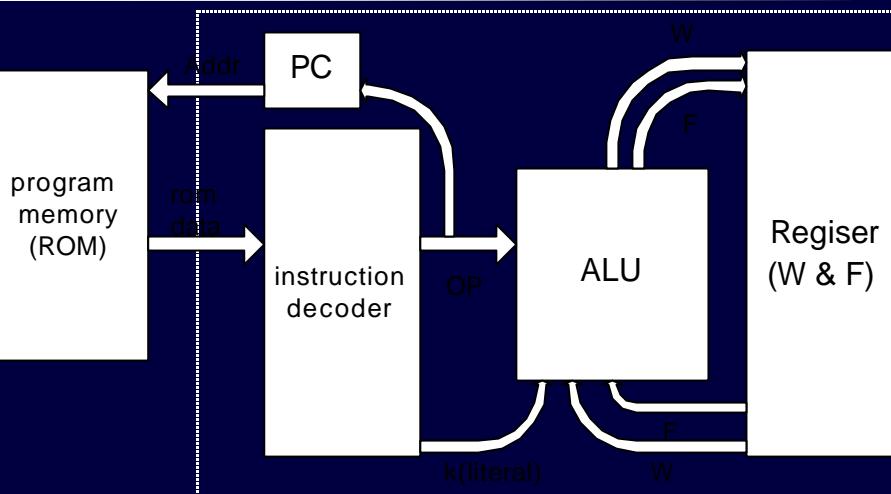

High Speed Digital Circuit Lab

4


Top module

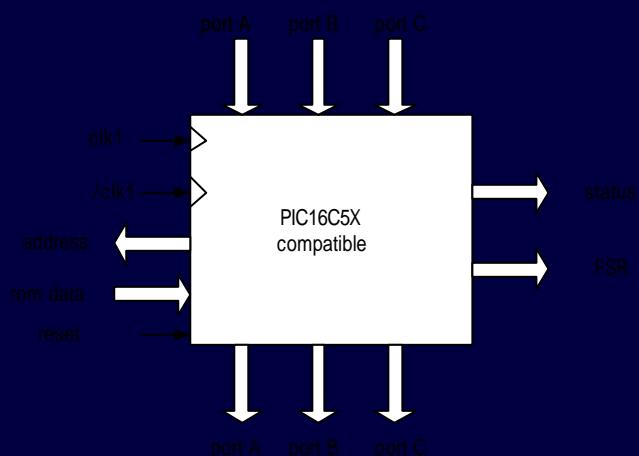

High Speed Digital Circuit Lab

5

Machine Cycle

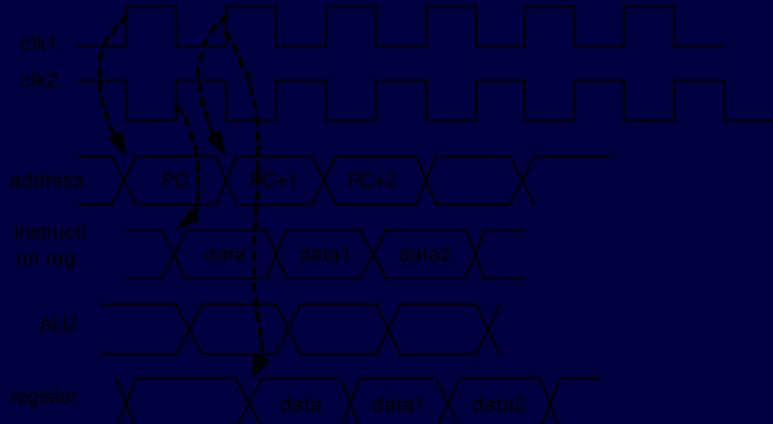

High Speed Digital Circuit Lab

6

Instruction Decoder

- Instruction_decoder_top
 - instruction register
 - instruction decoder
 - mux carry, zero write
 - mux few
 - mux indirect addressing



High Speed Digital Circuit Lab

7

Instruction register

```
always @(posedge clk or posedge reset) begin
    if( reset == 1'b1)
        inst_buf <= 12'b0000_0000_0000;
    else begin
        if/*call_inst == 1'b1 || goto_inst == 1'b1 */ skip == 1'b1)
            inst_buf <= 12'b0000_0000_0000;
        else
            inst_buf <= rom_data;
    end
end
assign inst = inst_buf;
assign k = inst_buf[7:0];
assign longk = inst_buf[8:0];
assign fsel = (inst_buf[4:0] === 4'b0000) ? fsl_rs:inst_buf[4:0];
assign d = inst_buf[5];
```



Instruction decoder

```
assign op_nop = (inst[11:0] == NOP) ? 1 : 0;
assign op_movwf = (inst[11:5] == MOVWF) ? 1 : 0;
assign op_clrw = (inst[11:0] == CLRW) ? 1:0;
assign op_clrf = (inst[11:5] == CLRF) ? 1:0;
assign op_subwf = (inst[11:6] == SUBWF) ? 1:0;
assign op_decf = (inst[11:6] == DECF) ? 1:0;
.
.
.
assign op_andlw = (inst[11:8] == ANDLW) ? 1:0;
assign op_xorlw = (inst[11:8] == XORLW) ? 1:0;
```



Mux_few, mux_cz_write

- assign few = (op_clrf == 1) ? 1 :
 (op_movwf == 1) ? 1 :
 (op_bcf == 1) ? 1:
 (op_bsfc == 1) ? 1:
 (op_subwf == 1 && d == 1) ? 1:
 (op_decf == 1 && d == 1) ? 1
- assign z_write = (op_clr == 1 ||
 op_clrf == 1 ||
 op_subwf == 1 ||)
- assign c_write = (op_subwf == 1 ||
 op_addwf == 1 ||
 op_rrf == 1 ||)



Program Counter

- Normal Instruction: pc = pc + 1
- Branch instruction - CALL, GOTO, RETLW
 - Next literal address or popped address from stack1 or 2
- SKIP?? - DECFSZ, INCFSZ, BTFSC, BTFSS
 - Insert NOP instead of prefetched instruction.



Program Counter (cont.)

```
always @(posedge clk or posedge reset) begin
    ...
    else begin
        if(op_goto == 1) begin
            pc[8:0] <= longk; pc[10:9] <= status_pa;
        end
        else if(op_call == 1) begin
            .....
            pc[7:0] <= k;   pc[8] <= 0;   pc[10:9] <= status_pa;
        end
        else if(op_retlw == 1) begin
            .....
        end
        else if((fwe == 1) && (fsel == 5'b000010)) begin
            pc[7:0] <= fin;
        end
    end
.....
```



ALU

- mux_alu_a
 - f or k or w. Default: w
- mux_alu_b
 - f or k or w or 1. default :f
- alu_op_gen
- alu_op



ALU_OP_GEN

```
assign alu_op =
    (op_addwf == 1 || op_incf == 1 || op_incfsz == 1) ? ALU_ADD:
    (op_subwf == 1 || op_decf == 1 || op_decfsz == 1) ? ALU_SUB :
    (op_andlw == 1 || op_andwf == 1) ? ALU_AND :
    (op_iorwf == 1 || op_iorlw == 1 || op_movwf == 1 || op_movf == 1 ||
     op_movlw == 1 || op_retlw == 1) ? ALU_OR :
    (op_xorwf == 1 || op_xorlw == 1 || op_clrw == 1 || op_clrf == 1) ? ALU_XOR :
    (op_comf == 1) ? ALU_COM :
    (op_rrf == 1) ? ALU_RR:
    (op_rlf == 1) ? ALU_RL:
    (op_swapf == 1) ? ALU_SWAP:
    (op_bcf == 1) ? ALU_BC:
    (op_bsf == 1) ? ALU_BS:
    (op_btfsc == 1) ? ALU_BTC:
    (op_btfss == 1) ? ALU_BTS:
    4'b1111;
```



ALU_OP

```
always @(op or a or b or carry_in or bitdecode) begin
    case (op)
        ALU_ADD: out <= a+b;
        ALU_SUB: out <= a-b;
        ALU_AND: out <= {1'b0, a & b};
        ALU_OR: out <= {1'b0, (a | b)};
        ALU_XOR: out <= {1'b0, (a ^ b)};
        ALU_COM: out <= {1'b0, ~a};
        ALU_RR: out <= {a[0], carry_in, a[7:1]};
        ALU_RL: out <= {a[7:0], carry_in};
        ALU_SWAP: out <= {1'b0, a[3:0], a[7:4]};
        ALU_BC: out <= {1'b0, a & (~bitdecode)};
        ALU_BS: out <= {1'b0, a | bitdecode};
        ALU_BTC: out <= {1'b0, a & bitdecode};
        ALU_BTS: out <= ((a & bitdecode) != 8'b0000_0000) ? 9'b0_0000_0000 : {carry_in, a};
        default : out <= {carry_in, a};
    endcase // case(op)
```



Registers

- Special Function Register
 - INDF, STATUS, FSR, PORT A,B,C
- Register File

FSR<6:5>	00	01	10	11
00	INDF			
01	TMR0			
02	PCL			
03	STATUS			
04	FSR			
05	PORT A			
06	PORT B			
07	PORT C			
08	General Purpose Register	2Fh	4Fh	6Fh
0F		10h 1Fh	30h 3Fh	50h 5Fh
				70h 7Fh



Registers (cont.)

- Mux_reg_w, Mux_reg_f
 - Input of W register and register file
- Reg_w, reg_general, reg_status, reg_fsr reg_io



Register File

- assign reg_addr = (fsel == 5'b00000) ? fsr[4:0]: fsel;
- assign bank_addr = fsr[6:5];
- always @(posedge clk_q4) begin
- if(fwe == 1) begin
- if(reg_addr > 15) begin
- case (bank_addr)
- 2'b00:gpr0[reg_addr] <= fin;
- 2'b01:gpr1[reg_addr] <= fin;
- 2'b10:gpr2[reg_addr] <= fin;
- 2'b11:gpr3[reg_addr] <= fin;
- endcase
- end
- else if(reg_addr > 7) gpr[reg_addr] <= fin;
- end // if (fwe == 1)
-



Verification

- Instantiation UUT
- Stimuli and response
- Clock Generator

➡ Verify using test assembly programs.



Verification(cont.)

- Stimuli

```
assign rom_data = rom[rom_addr];
initial begin
    reset =0;
    pa_in=8'haa;
    pb_in=8'hbb;
    pc_in=8'hcc;
    #2 reset =1;
    #2 reset =0;
    $readmemb("rom.dat", rom);
    #5020
    pa_in = 8'h55;
    #5030
    pa_in = 8'hAA;
end
```



High Speed Digital Circuit Lab

20

Verification (cont.)

- always begin

```
#100 clk_q1=0; clk_q2=1;
#100 clk_q1=1; clk_q2=0;
end
```

- always @ (posedge clk_q1 or posedge clk_q2) begin

```
$display($time,, "%d fsr:%b status:%b f_out:%h %b %h %b %d", clk_q1,
        fsr_out, status_out, f_out, pa_in, pb_out, rom_data, rom_addr);
end
```



High Speed Digital Circuit Lab

21

Verification (cont.)

- 100 0 1 0 101000000000 10101010 00000000 00000000 00000000 111111111111 GOTO fetch
- 200 1 0 0 101000000000 10101010 00000000 00000000 00000000 111111111111
- 300 0 1 0 101000000000 10101010 00000000 00000000 00000000 111111111111
- 300 0 1 0 101000000000 10101010 00000000 00000000 00000000 000000000000
- 300 0 1 0 000001101010 10101010 00000000 00000000 00000000 000000000000
- 400 1 0 0 000001101010 10101010 00000000 00000000 00000000 000000000000
- 500 0 1 0 000001101010 10101010 00000000 00000000 00000000 000000000000
- First instruction fetch(CLRF)
- 8000 1 0 0 000000100110 01010101 00000000 00000101 00000000 00000010111
- 8100 0 1 0 000000100110 01010101 00000000 00000101 00000000 00000010111
- 8100 0 1 0 000000100110 01010101 00000110 00000101 00000000 00000011000 Port B output : 06 !!!



Synthesis(XILINX spartan S40PQ240)

- Total accumulated area :
- Number of BUFG : 2
- Number of CLB Flip Flops : 680
- Number of CY4 : 12
- Number of FG Function Generators : 798
- Number of H Function Generators : 270
- Number of IBUF : 37
- Number of OBUF : 67
- Number of Packed CLBs : 411
- Number of ports : 106
- Number of nets : 2011
- Number of instances : 1881
- Number of references to this view : 0

