


Summer 2001 – Test 1 Solutions

1. (10 pts) Write a single process that will function as a clock divide-by-2 function. You can use any approach that you desire (with or without a sensitivity list). The new clock signal should be called *clkhalf* and the input clock signal is called *clk*. Use *std_logic* for the signal types and assume that the clock only has values of '1' and '0'. You CANNOT assume that the duty cycle is 50%.

```
signal clkhalf : std_logic := '0';
process (clk)
begin
    if (clk = '1') then clkhalf <= not (clkhalf);
    end if;
end process;
```

2. Write a VHDL code segment that models the situation shown below. The signal declarations are as shown. When neither tri-state buffer is enabled, the Y value should be a weak '1' condition, and if both tri state buffers are enabled then Y should be a strong unknown.

Signal TA, A, TB, B, Y : std_logic;

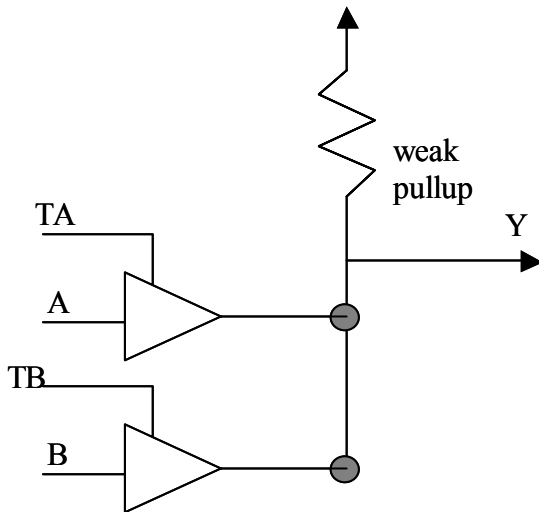

-- use multiple driver approach

```
Y <= 'H'; -- pullup
Y <= A when (TA = '1') else 'Z';
Y <= B when (TB = '1') else 'Z';
```

When tristate control is '1', then output follows input
else high impedance output.

3. (15 pts) a. Draw the waveform generated by the following code:

SEE ATTACHED FIGURE ('a3' waveform)

```
architecture A of E
begin
  signal a: std_logic = 'Z';

  a <= transport 'H' after 3 ns;
  a <= transport 'L' after 5 ns;
  a <= transport '0' after 7ns;

end E;
```

4. (10 pts) Draw the waveform generated by the following process for at least 20 ns. ('wait on' waits for an event on the specified signal).

SEE ATTACHED FIGURE ('a4' waveform)

```
signal A: std_logic:= '0';
process
begin

  A <= transport '1' after 5 ns;
  wait on A;
  A <= transport '0' after 5 ns;
  Wait on A;
End process;
```

5. (10 pts) Draw the waveform generated by the following process for at least 20 ns.

SEE ATTACHED FIGURE ('a5' waveform)

```
signal A: std_logic:= '0';
process
begin

  A <= transport '1' after 5 ns;
  wait on A;
  A <= transport '0' after 5 ns;
  Wait;
End process;
```

6. (10 pts) Draw the waveform generated by the following process for at least 20 ns.

SEE ATTACHED FIGURE ('a6' waveform)

```
signal A: std_logic:= '0';
process
begin

    A <= transport '1' after 5 ns;
    wait on A;
    A <= transport '0' after 5 ns;
End process;
```

7. (10 pts) Draw the waveform generated by the following process for at least 20 ns.

SEE ATTACHED FIGURE ('a7' waveform)

```
signal A: std_logic:= '0';
process
begin

    A <= transport '1' after 5 ns;
    wait for 2 ns;
    A <= transport '0' after 2 ns;
    Wait;
End process;
```

8. (15 pts) Draw the waveforms generated by the following VHDL code fragment for at least 20 ns.

(Hint: recall the difference between inertial and transport delay models).

SEE ATTACHED FIGURE ('a8', 'b8', 'c8' waveforms)

```
signal A, B, C: std_logic:= '0';

    A <= transport '1' after 4 ns, '0' after 6 ns;
    B <= transport A after 3 ns;
    C <= A after 3 ns;
```

9. (10 pts) In the process below, what is the value of 'cnt' at time = 25 ns? EXPLAIN your answer to get partial credit.

SEE ATTACHED FIGURE ('a9', 'b9') CNT = 4 because the process is triggered twice on assignments to A, B.

```
Signal A, B : std_logic := '0';
```

```
Process (A, B)
```

```
Variable cnt: = 0;
```

```
Variable ll :line;
```

```
Variable init :boolean
```

```
Begin
```

```
  If (init = FALSE) then
```

```
    Init := TRUE;
```

```
  Else
```

```
    Cnt := cnt + 1; -- do not increment CNT for initial triggering of process
```

```
  End if;
```

```
  A <= transport not(A) after 10 ns;
```

```
  B <= transport A;
```

```
End process;
```

10. Write a VHDL process that will generate a fixed number of clock cycles based upon a generic called 'CLKNUM'. The clock is a 50% duty cycle clock whose period is a generic called 'CLKPER'. The initial value of the clock signal should '0' and the clock signal name is 'clk'.

```
Signal clk: std_logic;
```

```
process
```

```
begin
```

```
  for i in 0 to CLKNUM-1 loop
```

```
    wait for CLKPER/2;
```

```
    clk <= not(clk);
```

```
    wait for CLKPER/2;
```

```
    clk <= not(clk);
```

```
  end loop;
```

```
  wait;
```

```
end process;
```

11. (10 pts) Assume that 'clk' is a 50% duty cycle clock with a 10 ns period.

a. In the process below, what is the value of 'atime' ? **0 because process triggers on clk.**

```
Process (clk)
Variable atime: time;

    Atime := clk'last_event;
End process;
```

b. In the process below, what is the value of 'atime' ? **5 ns (trigger on each clk change)**

```
Process (clk)
Variable atime: time;

    Atime := clk'delayed'last_event;
End process;
```

12. (5 pts) Given a signal 'A', what would need to be in the sensitivity list of a process if I wanted the process to be triggered each time an ASSIGNMENT was made to 'A'?

A' TRANSACTION

13. (5 pts) What is difference between *std_logic* and *std_ulogic* data types? When would I use one over the other?

Std_logic is the resolved version of std_ulogic. You would use std_logic for signals that need multiple drivers, and either std_logic or std_ulogic if the signal only has one driver.

